


Physical Science 430-2008

Pretest 3.3

1. The heating element of an electric stove has a resistance of $50\ \Omega$. It is connected to a power source of $220\ \text{V}$ and turned on for 2.0 minutes.


What is the current which flows through this heating element?

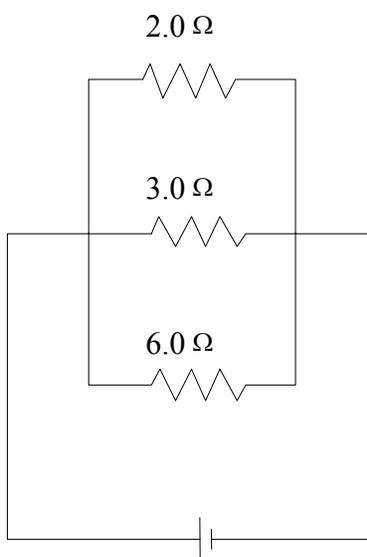2. Three known resistances are connected in parallel to the terminals of a power source. The current passing through the $3.0\ \Omega$ resistance is $1.0\ \text{A}$.




What is the intensity of the current coming from the power source?

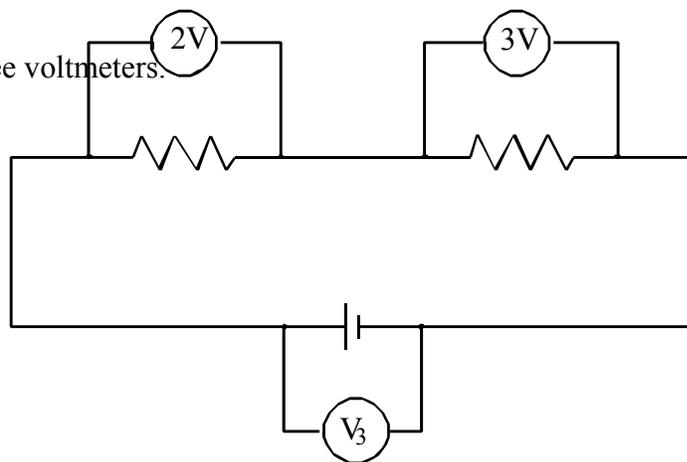3. Given the following electric circuit with three voltmeters. What is the reading on voltmeter V_3 ?




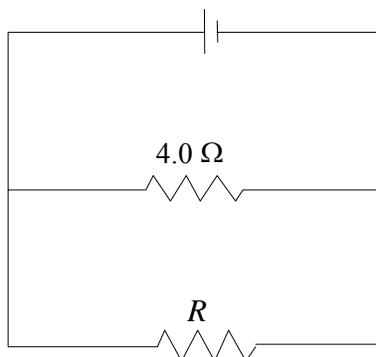4. In the following electric circuit, one of the two resistances is 4.0Ω . The other resistance, " R ", is unknown. The voltage of the power source is 12 V and the electric current from the source is 4.5 A .



What is the value of resistance " R "?

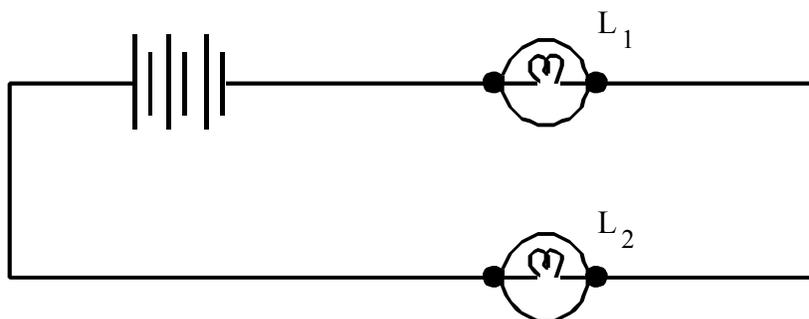
5. The diagram below represents an electric circuit consisting of batteries and two identical light bulbs.



The potential difference across light bulb L_2 is _____.

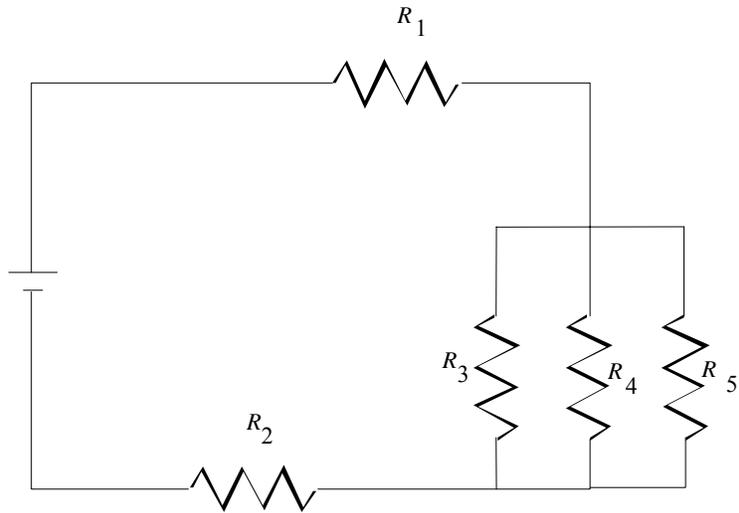- A) the same as that across the terminals of the batteries.
- B) twice that across light bulb L_1 .
- C) half that across light bulb L_1 .
- D) the same as that across light bulb L_1 .


- 6 You must build a circuit equivalent to the one below but with only one resistor. What would be the value of its resistance?




$$R_1 = 25 \Omega \quad R_2 = 15 \Omega \quad R_3 = 20 \Omega$$

$$R_4 = 30 \Omega \quad R_5 = 60 \Omega$$

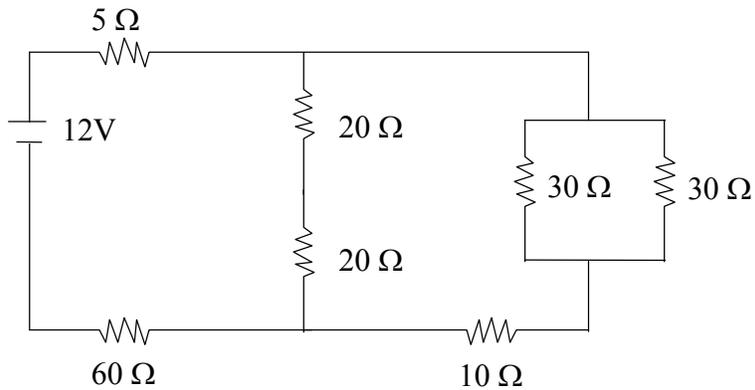
- 7 What is the voltage across each of the 20Ω resistors? The total voltage of the circuit is 12 V .



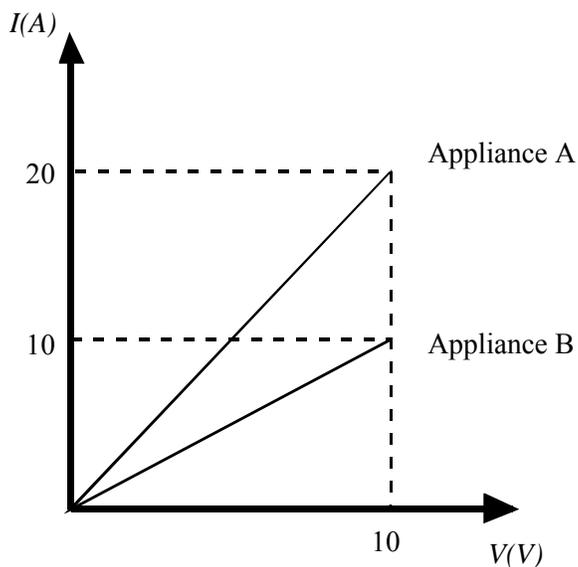8. Which appliance has greater conductance? (see graph) Explain.



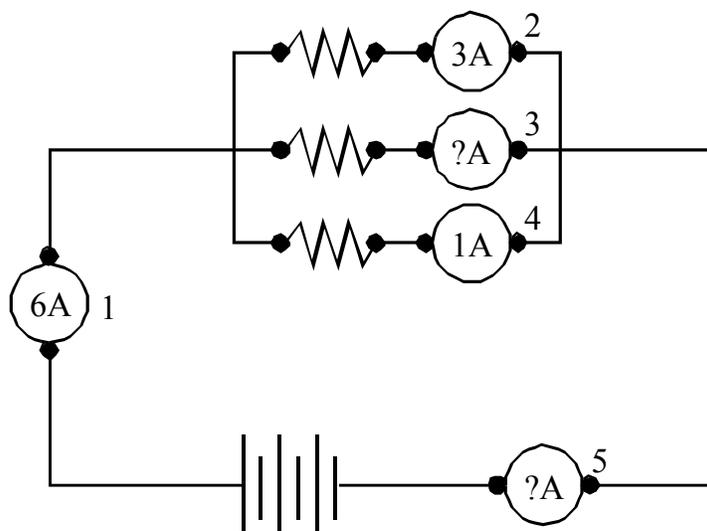9. The electric circuit in the diagram below consists of 3 resistors and 5 ammeters numbered 1 to 5.



What are the readings of ammeter 3 and ammeter 5?

10. Pauline is repairing her radio. She needs to replace a $250\ \Omega$ resistor that has burnt out. There are only $100\ \Omega$ resistors available. Draw a circuit diagram to suggest a way that they can be used to replace the burnt resistor.¹

¹ Flashback topics: naming simple ionic and covalent compounds (no polyatomics; no transition metals). Calculating g/L.

ANSWERS

1. $V = IR$
 $220 = I(50)$
 $I = 220/50 = 4.4A$

2. Since V is constant, $V = I_2R_2$
 $V = 1A(3\Omega) = 3V$
 $I_1 = V/R_1 = 3/2 = 1.5A$
 $I_3 = V/R_3 = 3/6 = 0.5A$

$$I_T = I_1 + I_2 + I_3$$
$$= 1 + 1.5 + 0.5 = 3A.$$

Another way:

Since V is constant, $V = I_2R_2$
 $V = 1A(3\Omega) = 3V$

Get total resistance: $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$
 $1/R_T = 1/2 + 1/3 + 1/6$
 $1/R_T = 3/6 + 2/6 + 1/6$
 $1/R_T = 6/6 = 1 \Omega.$
 $R_T = 1 \Omega$
 $V = I_T R_T$
 $3 = I_T (1)$
 $I_T = 3A$

3. $V_T = V_3 = V_1 + V_2$
 $= 2V + 3V = 5V$

4. $V = I_1R_1$
 $12 = I_1(4)$
 $I_1 = 12/4 = 3A$
But total current is $4.5A$, so $I_2 = 4.5A - 3A = 1.5A$

Since voltage is current in parallel,

$$R_2 = V/I_2 = 12/1.5 = 8 \Omega.$$

5. (D) same as L_1 , because they are identical lightbulbs. Note that it's a series circuit, so $V_1 + V_2 = V_T$

6.

$$1/R_p = 1/R_3 + 1/R_4 + 1/R_5$$

$$1/R_p = 1/20 + 1/30 + 1/60$$

$$1/R_p = 3/60 + 2/60 + 1/60$$

$$1/R_p = 6/60$$

$$R_p = 60/6 = 10 \Omega.$$

$$R_T = R_1 + R_p + R_2$$

$$= 25 + 10 + 15 = 50 \Omega.$$

7. The two parallel 30 Ω . resistors have an equivalent resistance of 15 Ω . They are in series with 10 Ω , giving them an equivalent of 25 Ω . But this equivalent of 25 Ω is parallel to the two 20 Ω guys (40 Ω in all), to produce a parallel resistance of:

$$1/R_p = 1/40 + 1/25$$

$$1/R_p = 5/200 + 8/200$$

$$1/R_p = 13/200$$

$$R_p = 200/13 = 15.38 \Omega.$$

$$R_T = 15.38 + 5 + 60 = 80.38 \Omega.$$

$$V_T = I_T R_T$$

$$12 = I_T (80.38 \Omega.)$$

$$I_T = 12/80.38 = 0.149 \text{ A}$$

This is the current arriving at the parallel branch before it splits up, where $R_p = 15.38 \Omega$. So the voltage for the parallel branch is $V_p = I R_p = 0.149 \text{ A} (15.38 \Omega.) = 2.30 \text{ V}$

So each 20 Ω resistor will experience $2.30 \text{ V} / 2 = 1.15 \text{ V}$.



Are you still there?

The conductance of appliance A is greater than that of appliance B because:

8.

- at the same point on the graph, the current intensity is greater for appliance A;
- the slope of the line is greater for appliance A;
- for the same voltage, the I/U ratio is greater for appliance A.

9. The readings of ammeter 3 and ammeter 5 are 2 A and 6 A, respectively.

10.

