

Solutions to Government Exam Questions

1. $R_T = [R_1^{-1} + R_2^{-1} + R_3^{-1}]^{-1} = [100^{-1} + 100^{-1} + 100^{-1}]^{-1} = 33.3 \Omega.$

2. A_c because it is the total current.

3. $V_T = IR_T$

$$9 = I(2 + 4 + 5 + 7)$$

$$I = 0.5 \text{ A}$$

4. Circuit M

$$V_T = IR_T$$

$$12 = I(3 + 9 + 12)$$

$$I = 0.5 \text{ A}$$

Circuit N needs 10 times the current, so we need $10(0.5 \text{ A}) = 5 \text{ A}$

Resistance? $V = IR$

$$12 = 5R$$

$$R = 2.4 \Omega.$$

Which two resistors will give 2.4Ω ?

Try them into the formula: $R_T = [R_1^{-1} + R_2^{-1}]^{-1} = [3^{-1} + 12^{-1}]^{-1} = 2.4 \Omega.$

Answer 3 Ω And 12 Ω .

5. Voltage is constant! Answer 12 V

6. C

7. $V_T = IR_T = 0.25(10 + 20 + 40) = 17.5 \text{ V}.$

8. $I_T = 0.75 + 0.75 = 1.5 \text{ A}$

9. If the resistance at the second bulb is twice as big, then it will draw only half the current.
 $0.5(0.6) = 0.3 \text{ A}.$

Attach an ammeter to L_2 to check if this is the case.