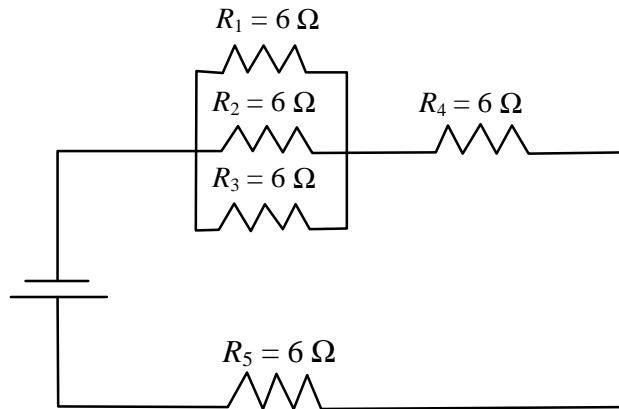



Combination Circuits: for 430 eyes only

- 1 Determine the equivalent resistance (R_{eq}) of the following circuit.




$$\begin{aligned} (1/R_p) &= 1/6 + 1/6 + 1/6 \\ R_p &= 6/3 = 2 \Omega. \\ R_t &= R_p + R_4 + R_5 \\ &= 2 + 6 + 6 = 14 \Omega. \end{aligned}$$

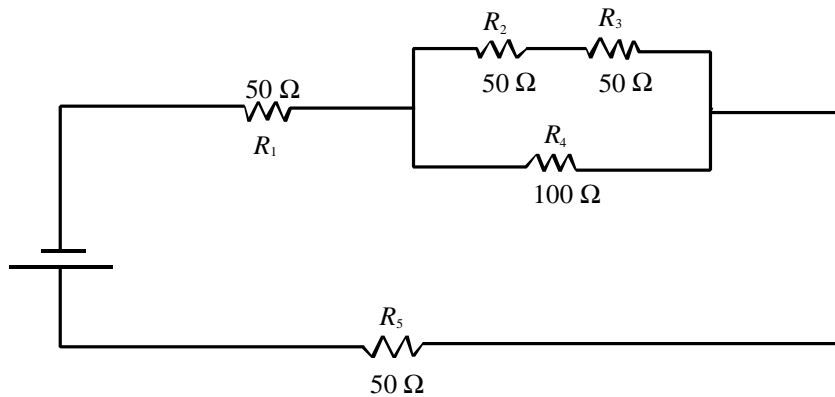- 2 The following circuit consists of a power supply and five resistors (R_1 , R_2 , R_3 , R_4 and R_5). Find R_t .



$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{R_2 + R_3} + \frac{1}{R_4} \\ 1/R_p &= (1/100) + (1/100) \\ R_p &= 50 \Omega. \\ R_t &= R_1 + R_p + R_5 = 50 + 50 + 50 = 150 \Omega. \end{aligned}$$

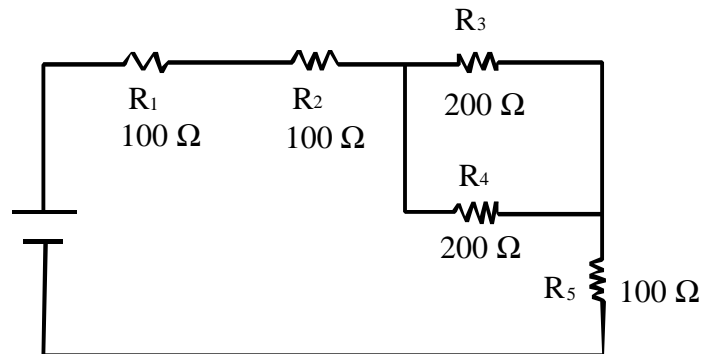- 3 The following circuit consists of a power supply and five resistors (R_1 , R_2 , R_3 , R_4 and R_5). What is the equivalent resistance of the entire circuit (R_{eq})?




$$(1/R_p) = (1/200) + (1/200)$$

$$R_p = 100 \Omega.$$

$$R_t = R_1 + R_2 + R_p + R_5 = 100 + 100 + 100 + 100 = 400 \Omega.$$

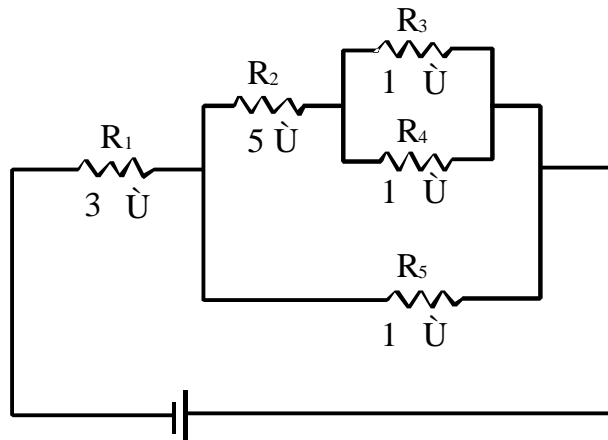- 4 The following electric circuit consists of a power source and five resistors (R_1 , R_2 , R_3 , R_4 and R_5).



What is the equivalent resistance, R_{eq} , of this circuit?

$$(1/R_{ptop}) = R_2 + (R_3^{-1} + R_4^{-1})^{-1} = 5 + (1^{-1} + 1^{-1})^{-1}$$


$$R_{ptop} = 5.5 \Omega.$$

$$(1/R_p) = 1/R_{ptop} + 1/R_5 = 1/5.5 + 1/1$$

$$R_p = 0.85 \Omega.$$

$$R_t = R_1 + R_p = 3 + 0.85 = 3.85 \Omega.$$

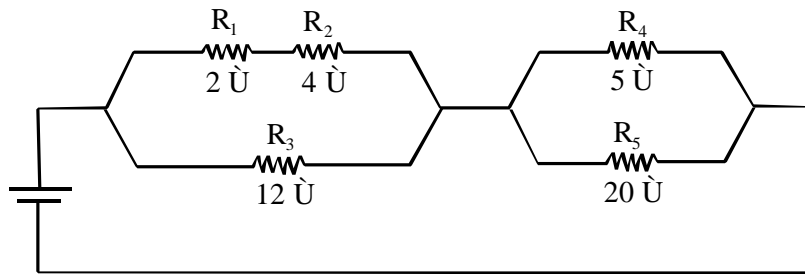5 The following circuit consists of five resistors (R_1 , R_2 , R_3 , R_4 and R_5).



What is the voltage drop across R_5 if the total voltage is 20 V?

$$\frac{1}{R_{\text{left}}} = \frac{1}{2 + 4} + \frac{1}{12}$$

$$R_{\text{left}} = 4 \Omega.$$

$$1/R_{\text{right}} = 1/5 + 1/20$$

$$R_{\text{right}} = 4 \Omega.$$


Since the resistances are equal each will experience a voltage drop of $20 \text{ V}/2 = 10 \text{ V}$.

Otherwise, you'd have to do this:

$$\begin{aligned} V_t &= IR_t \\ 20 &= I(4 + 4) \\ I &= 2.5 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{\text{right}} &= V_5 = IR_{\text{right}} \\ &= 2.5(4) = 10 \text{ V}. \end{aligned}$$

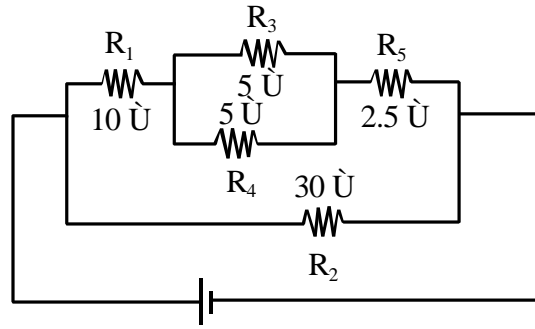- 6 The following electric circuit consists of a power source and five resistors (R_1 , R_2 , R_3 , R_4 and R_5).



What current flows through R_4 if the total voltage is 32 V?

$$1/R = 1/5 + 1/5$$


$$R = 2.5 \Omega. \text{ (for little parallel part)}$$

$$\frac{1}{R_p} = \frac{1}{R_1 + R + R_5} + \frac{1}{R_2} = \frac{1}{15} + \frac{1}{30}$$

$$R_p = 30/30 = 10 \Omega.$$

$$I_{top} = V/R_{top} = 32/15 = 2.133 \text{ A, but then it splits within the little parallel part, so } I_4 = 2.133/2 = 1.07 \text{ A.}$$

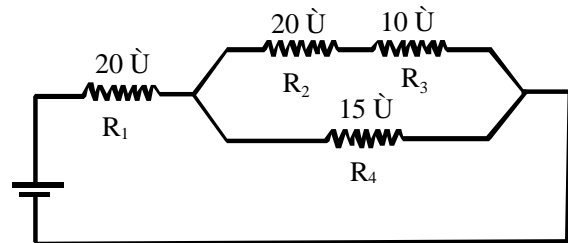- 7 A series-parallel electric circuit is illustrated on the right.



What current flows through R_2 if $V_t = 100 \text{ V}$?

$$1/R_p = 1/(20+10) + 1/15$$

$$R_p = 10 \Omega.$$

$$R_t = R_p + R_1 = 10 + 20 = 30 \Omega.$$


$$V = I_t R_t$$

$$100 = I_t (30)$$


$I_t = 3.33 \text{ A}$. But the parallel part has a resistance of 10Ω . Its voltage drop =

$V = IR = 3.33(10) = 33.3 \text{ V}$. So the top part of the parallel branch will receive $33.3 \text{ V} / 30 \Omega = 1.11 \text{ A}$. (why divide by 30Ω ? It's the resistance for the top part of the parallel branch)

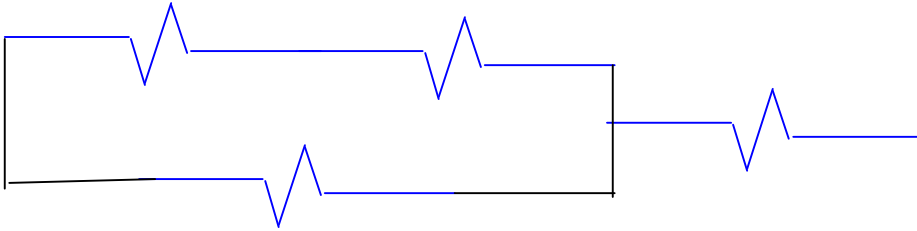
8 How do you connect four 1.00Ω resistors so that the total resistance is 1.67Ω ?



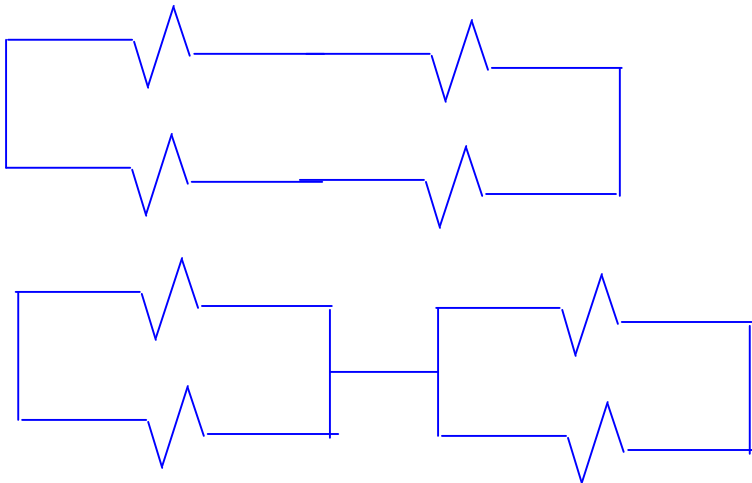9 Find TWO ways of connecting four 2.0Ω resistors so that their total resistance is 2.0Ω .



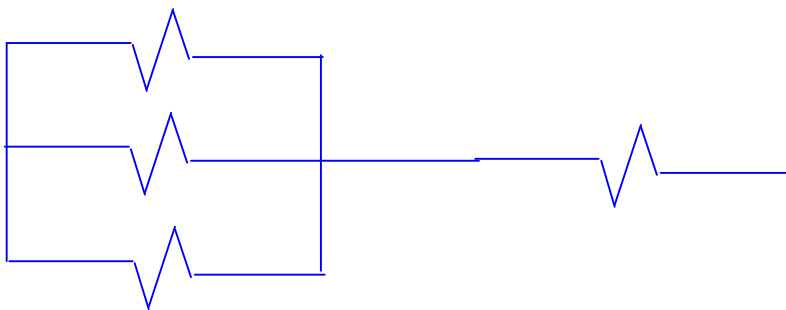10 Three different resistors (A, B and C) have an identical voltages of 3.0 V . The fourth resistor has a potential difference of 4.0 V . Draw a circuit that would be consistent with the above measurements, and then find the total voltage.



$$V_t = V_p + V_4 = 3 + 4 = 7 \text{ V}$$

