

Combination Circuits

Think Tank

- Four *identical* resistors are connected to each other in some unknown way. The following voltages are measured:

$$V_t = 12 \text{ V}$$

$$V_1 = 12 \text{ V}$$


$$V_2 = 4 \text{ V}$$

$$V_3 = 4 \text{ V}$$

$$V_4 = 4 \text{ V}$$

Draw a circuit consistent with these results.

Solution:

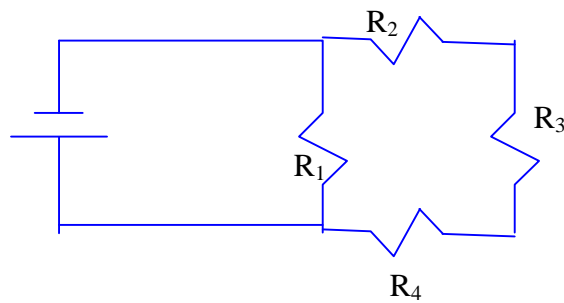


R₂, R₃ and R₄ are in series. Being identical resistors, they have the same voltage, so since $V_2 + V_3 + V_4 = V_t$

$$3V_2 = 12$$

$$V_2 = 12/3 = 4 \text{ V}$$

The trio of resistors is parallel to R₁, so their combined voltage of 12 V equals that of R₁.

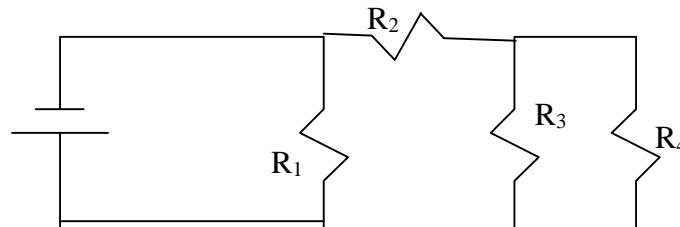- Four identical resistors are connected as shown in the diagram below:



If the total voltage is 12V, find the voltage across each resistor.

Solution:

R_1 experiences the total voltage. $V_1 = 12\text{V}$.

R_3 and R_4 are parallel to each other, and since they're identical, their combined resistance is half of any individual resistance such as R_2 . Since voltage is directly proportional to resistance, $V_2 = 2V_3$.

Also since R_2 is in series with the combined parallel branch consisting of R_3 and R_4 , and since R_1 is in parallel with the rest,

$V_2 + V_3 = V_1$. Substituting:

$$2V_3 + V_3 = 12$$

$$V_3 = 4 \text{ V. (and } V_4 = 4 \text{ V.)}$$

$$V_2 = 2(4) = 8 \text{ V}$$